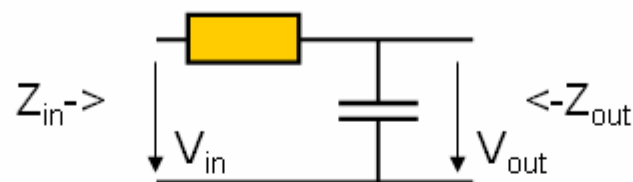


# Note to earlier lecture: LP-filter is an approximation of the ideal integrator



$$H(f)V_{in}(f) = V_{out}(f)$$

$$H(f) = \cancel{I(f)}Z_{out}(f) / [\cancel{I(f)}Z_{in}(f)] = Z_{out}(f) / Z_{in}(f)$$

$$H(f) = \frac{(j\omega C)^{-1}}{R + (j\omega C)^{-1}} = \frac{1}{j\omega RC + 1}$$

$$H(f) \approx \frac{1}{j\omega RC}, \omega \gg 1$$

Ideal integrator is defined by

$$V_{out}(f) = \mathcal{F} \left[ \int_{-\infty}^t v_{in}(\lambda) d\lambda \right] = \frac{V_{in}(f)}{j2\pi f} + \frac{1}{2}V_{in}(0)\delta(f)$$

$$V_{out}(f) \Big|_{V_{in}(t)=\delta(t)} = \frac{1}{j2\pi f} + \frac{1}{2}\delta(f)$$

$$\mathcal{F}[\delta(t - \tau_d)] = \exp(-j\omega\tau_d)$$